

# Digital IC Design

## Exercise 5

### Clock Gating

**Professor Po-Tsang Huang**

**International College of Semiconductor Technology  
National Yang Ming Chiao Tung University**





# Power Analysis of sequential circuits

---

- Use the PrimePower to measure the power of a 3x3 convolution kernel provided by TA
  - ◆ Using clock gating
  - ◆ Without using clock gating
- Draw the architectures of 3x3 convolution kernels, and analysis and discuss the **power consumption & critical path** when using and without using clock gating.
 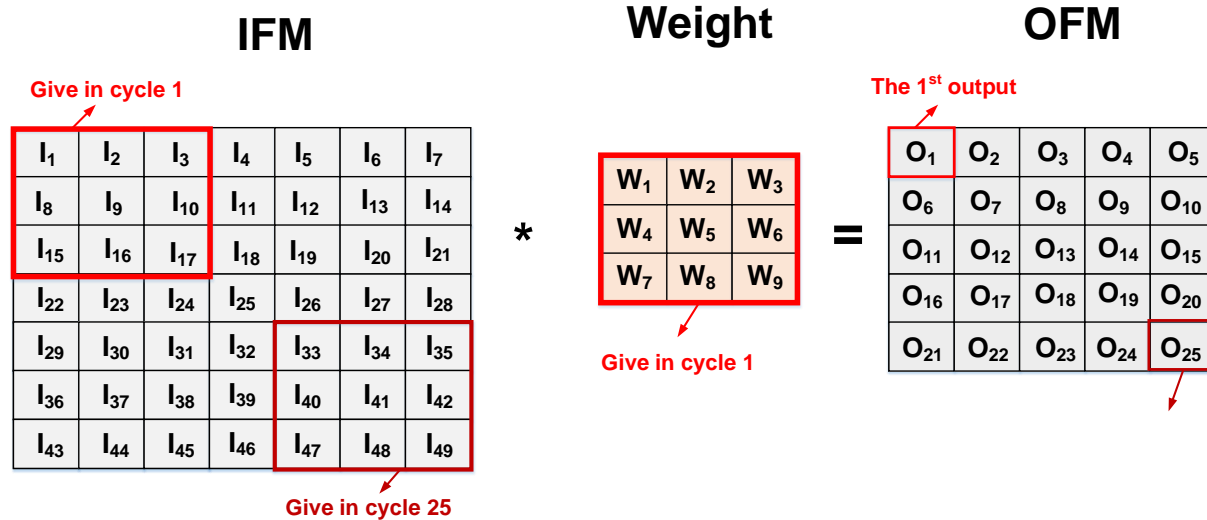
# Example

- $\text{In\_IFM} = 0 \rightarrow \text{Enable} = 1$
- $\text{In\_IFM} \neq 0 \rightarrow \text{Enable} = 0$



# Submission of Exercise-5

---

- Please upload the following files
  - ◆ Due day: PM 11:55 on 12/29
  - ◆ Report.pdf