

# Digital IC Design

## Final Team Project 128-bit Adder Tree

Professor Po-Tsang Huang

International College of Semiconductor Technology  
National Yang Ming Chiao Tung University



# Design an Adder Tree


## ■ Spec:

### ◆ Inputs ( $A_1, A_2, \dots, A_{128}$ ):

- 128 \* 1bit
- The minimum sampling rate is 2 GHz.
- You can add any extra control signals for your design

### ◆ Output ( $O_8 - O_1$ ):

- 8 bits

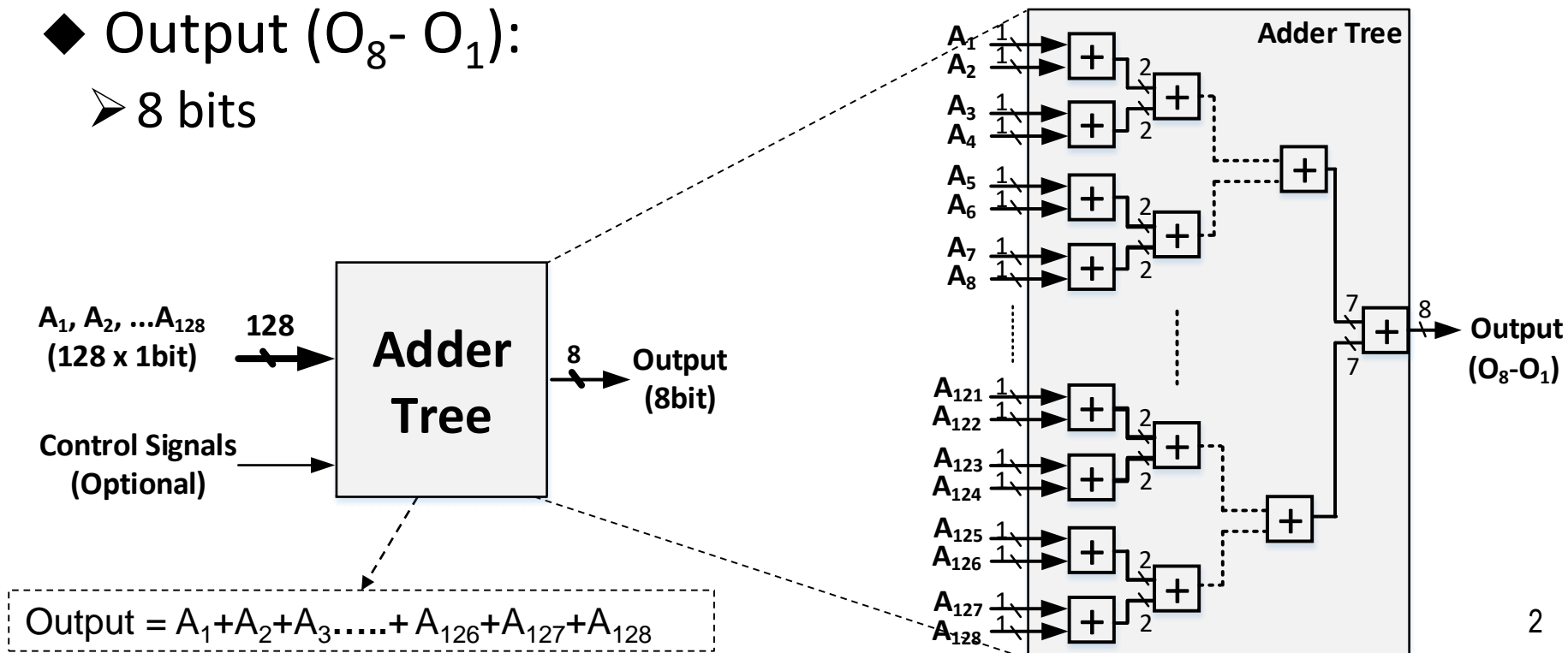

# Adder Tree



## Example:

◆ Inputs ( $A_1, A_2, \dots, A_8$ ):

➤ 8 \* 1bit

◆ Output( $O_4 - O_1$ ):

➤ 4bits

  

$$\text{Output} = A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8$$

